

OP-Amp :-

An Operational Amplifier or Op-Amps is a voltage amplifying device.

It is basically a multistage direct coupled high gain differential amplifier with high i/p impedance & low o/p impedance.

- It is used to amplify DC and AC signals.
 - It is a device that is used to amplify a signal using an external power source.
 - It amplifies the difference b/w two i/p signals applied across its i/p. Hence it is also called as difference amplifier.

- Op-Amps are generally composed of :-
Transistors, Resistors, Capacitors.

- Symbol :-

Inverting i/p V_1

Non-inverting i/p V_2


$+ V_{CC}$ + re supply

$- V_{EE}$ - re supply

V_0 o/p

V_D o/p

→ Pin details of Op-Amp :- (IC 741)

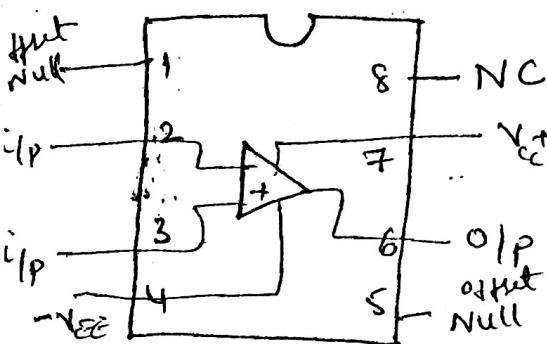

V_2 :- Non-inverting i/p

V_1 :- Inverting i/p

V_o :- o/p

+ V_{CC} :- positive power supply

- V_{EE} :- -ve -

$$V_{out} = \text{gain} (V_+ - V_-) \quad (\text{open loop})$$

$$= A_v (V_+ - V_-)$$

→ so if V_+ is greater than V_- , the o/p goes +ve

if V_- is greater than V_+ , the o/p goes -ve

if $V_2 = V_1$, no o/p

→ Typically A_v is very large value around 10,000.

→ variation of o/p voltage :-

$$\text{if } V_o = 0, \text{ then } V_o = A (V_2 - V_1)$$

$$= \underline{\underline{A}} V_1$$

so that o/p voltage is out of phase with i/p voltage. ∴ it is called as inverting i/p terminal.

if $V_1 = 0$, then


$$V_o = A_v (V_2 - V_1)$$

$$\underline{V_o} = \underline{A_v V_2}$$

i.e., o/p voltage is in phase with i/p voltage.

∴ it is called as non-inverting i/p.

* Ideal differential amplifier :-

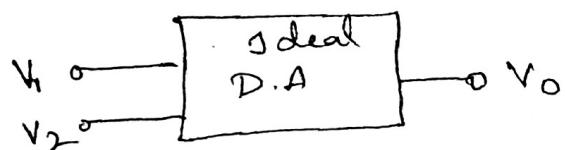

→ The fig shows the symbolic representation of differential amplifiers.

Let V_1, V_2 are the two i/p's, V_o is the o/p

∴ for an ideal op-amp the o/p voltage is directly proportional to diff b/w two i/p voltages.

$$\text{i.e., } V_o \propto (V_2 - V_1)$$

$$\therefore V_o = A (V_2 - V_1) \quad \text{--- (1)}$$

A → proportionality constant which is equal to gain of the D.A.


(3)

applies

i.e., from Eqn (1)

$$V_o = A_c (V_{2A} - V_1)$$

But $V_{2A} = V_1$

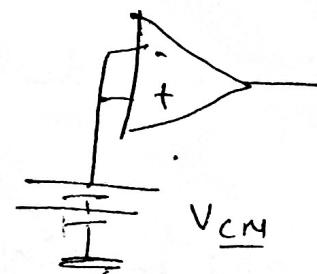

$$\therefore \underline{V_o = 0}$$

But the o/p voltage of practical amplifier not only depends on difference b/w two i/p voltages but also depends on the avg common level of the two i/p signals.

Such avg level of the two i/p signals is called as common mode signal (V_c).

$$\therefore V_c = \frac{V_1 + V_2}{2} \quad \text{--- (4)}$$

\therefore practically, the D.A produces the o/p voltage proportional to CMS. The gain which it amplifies the CMS to produce the o/p is called CM gain (A_c)

$$\therefore V_o = A_c V_c \quad \text{--- (5)}$$

$$\therefore A_c = \frac{V_o}{V_c} \quad \text{--- (6)}$$

The total o/p voltage of any d.a is expressed as sum of o/p voltage under differential mode & o/p voltage under common mode


olifiers

i.e., from Eqn ①

$$V_o = A_c (V_2 - V_1)$$

But $V_2 = V_1$

$$\therefore \underline{V_o = 0}$$

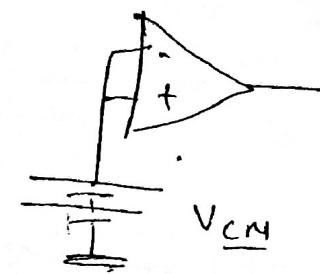

But the o/p voltage of practical amplifiers not only depend on difference b/w two i/p voltages but also depends on the avg common level of the two i/p signals.

Such avg level of the two i/p signals is called as common mode signal (V_c).

$$\therefore V_c = \frac{V_1 + V_2}{2} \quad \text{--- } ④$$

∴ practically, the D.A produces the o/p voltage proportional to CMS. The gain which it amplifies the CMS to produce the o/p is called CM gain (A_c)

$$\therefore V_o = A_c V_c \quad \text{--- } ⑤$$

$$\therefore A_c = \frac{V_o}{V_c} \quad \text{--- } ⑥$$

The total o/p voltage of any d.a is expressed as sum of o/p voltage under differential mode & o/p voltage under common mode

(3)

$$\therefore V_o = A_d V_d + A_c V_C$$

(7)

For ideal op-amp ; $A_d = \infty$ ($\because A_d = \frac{V_o}{V_d}$)

V_d is very small compared to V_o).

while $A_c = 0$ ($\because V_1 = V_2$)

→ Common Mode Rejection Ratio (CMRR):-

It is the ability of DA to reject the common mode signals.

It is defined as the ratio of differential mode gain to the common mode gain.

$$\text{i.e., } CMRR = \beta = \left| \frac{A_d}{A_c} \right|$$

Problems:-

(i) For a d.a with o/p voltages are 600 mV & 480 mV. The d.a gain of the amplifier is 10,000. Find the o/p voltage for the following CMRR (i) $CMRR = 200$ (ii) $CMRR = 10^6$

Soln:- $V_1 = 600 \mu V$; $V_2 = 480 \mu V$ & $A_d = 10000$

$$\therefore (i) CMRR = 200$$

$$CMRR = \beta = \left| \frac{A_d}{A_c} \right|$$

(8)

$$\therefore 200 = \frac{10000}{A_C}$$

$$A_C = 50$$

$$V_C = \frac{V_1 + V_2}{2} = \frac{(600 + 400) \mu V}{2} = \underline{\underline{540 \mu V}}$$

$$(iii) V_d = V_1 - V_2 = \underline{\underline{120 \mu V}}$$

$$\begin{aligned}\therefore V_o &= A_d V_d + A_c V_C \\ &= (10,000 + 120 \mu) + (50 \times 540 \mu V) \\ &= \underline{\underline{1222 \mu V}} \text{ or } \underline{\underline{1.222 V}}\end{aligned}$$


$$(iv) CMRR = 10^8$$

$$A_C = 10^{-4}$$

$$V_C = 540 \mu V ; V_d = 120 \mu V$$

$$\therefore V_o = \underline{\underline{1.2 V}}$$

Ideal characteristics of an Op-Amp :-

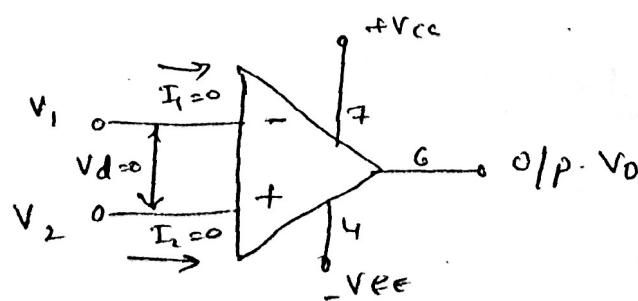

if we supply two o/p's to the two i/p terminals,
ideal op-amp draws no current ie, $I_1 = I_2 = 0$.
 \therefore i/p impedance $= \infty$

$$V_d = V_2 - V_1 = 0$$

It produces finite o/p voltage \therefore gain is ∞ .
The o/p V_o is ~~is~~ independent of Current drawn
from the o/p terminal. \therefore o/p impedance is ~~few~~ &
Can drive an infinite \approx of other ckts.

(a) Infinite voltage gain ($A_{OL} = \infty$) :-

$$A_{OL} = \frac{\text{Finite o/p voltage}}{\text{Zero diff voltage}}$$

$$= \frac{V_o}{V_d} = \frac{V_o}{0} = \infty$$

(b) Infinite i/p Impedance ($R_{in} = \infty$)

$$I_1 = I_2 = 0$$

i.e., it indicates V_2 & V_1 are open ckt.
 \therefore open ckt impedance is high & it is approximated

(e) Zero o/p impedance ($R_o = 0$) :-

$$R_o = 0$$

(d) Zero off-set voltage ($V_{os} = 0$) :-

$$V_{os} = 0$$

The presence of small o/p voltage even when both the i/p voltages are at gnd potential . ie $V_1 - V_2 \neq 0$

(e) Infinite Bandwidth ($BW = \infty$) :-

$$BW = \infty$$

$f = 0 \text{ to } \infty \text{ Hz}$
 $\therefore \text{gain is const.}$

(f) CMRR (P) :-

$$\rho = \infty$$

(g) Slew rate :- (S)

It is defined as max rate of change of o/p voltage with time . It is expressed in $V/\mu\text{sec.}$

$$S = \frac{dV_o}{dt} / \underline{\text{max}}$$

$$= \underline{\infty}$$

(b) Effect of Temperature :-

The chara of ideal op-amp will not change with temperature.

(i) Power supply rejection ratio (PSRR) :-

It is also called as power supply sensitivity.
It is defined as the ratio of the change in Op offset voltage due to the change in ^{any one} supply voltage by keeping other constant.

i.e., if V_{EE} is const & due to change in V_{CC} ,
there is change in Op offset voltage then PSRR is

expressed as ,

$$PSRR = \frac{\Delta V_{ios}}{\Delta V_{CC}}$$

or $PSRR = \frac{\Delta V_{ios}}{\Delta V_{EE}}$

It is expressed as mV/V & its ideal value is zero.

Ques:

Given the base currents for the emitter coupled transistors of PA_1 is $15 \mu\text{A}$ & $20 \mu\text{A}$, determine the i/p bias current (I_b) & I_{ios} .

Soln:- $I_{b1} = 15 \mu\text{A}$; $I_{b2} = 20 \mu\text{A}$

$$\therefore I_b = \frac{|I_{b1}| + |I_{b2}|}{2} = 17.5 \mu\text{A}$$

$$I_{ios} = |I_{b2} - I_{b1}| = 5 \mu\text{A}$$

Q2) For an op-Amp, the I_{ios} is 30nA while $I_b = 60 \text{nA}$. Calculate two i/p bias currents.

Soln:- $I_{ios} = |I_{b2} - I_{b1}|$; $I_b = \frac{I_{b1} + I_{b2}}{2} = 60 \text{nA}$

$$\stackrel{= 30 \text{nA}}{\longrightarrow} \quad I_b = I_{b1} + I_{b2} = 120 \text{nA} \quad - (2)$$

$$30 \text{nA} = I_{b2} - I_{b1}$$

$$I_{b2} = 30 \text{nA} + I_{b1} \quad - (3)$$

Substitute (3) in (2)

$$120 \text{nA} = I_{b1} + 30 \text{nA} + I_{b1}$$

$$2I_{b1} = 90 \text{nA}$$

$$I_{b1} = 45 \text{nA}$$

$$\therefore I_{b1} + I_{b2} = 120 \text{nA}$$

$$I_{b2} = 120 - I_{b1}$$

$$= (120 - 45) \text{nA}$$

$$= 75 \text{nA}$$

(j) :- S/Ip bias current (I_b) :-

$$I_b = \frac{|I_{b1}| + |I_{b2}|}{2}$$

$$\underline{I_b = 0}$$

(k) S/Ip offset current (I_{ios}) :-


$$I_{ios} = |I_{b2} - I_{b1}|$$

$$\underline{I_{ios} = 0}$$

Comparison b/w ideal & practical op-amp (MATU) :-

<u>Chera</u>	<u>Ideal</u>	<u>practical</u>
1. AOL	∞	2×10^5
2. Z_{in} or R_{in}	∞	$2 M\Omega$
3. Z_{out}	0	75Ω
4. V_{ios}	0	2mV
5. B.W	∞	19Hz
6. CMRR	∞	90dB
7. Slew rate	∞	0.5V/ μ s
8. I_b	0	80nA
9. I_{ios}	0	200nA

Block-diagram of IC - Op-amp :-

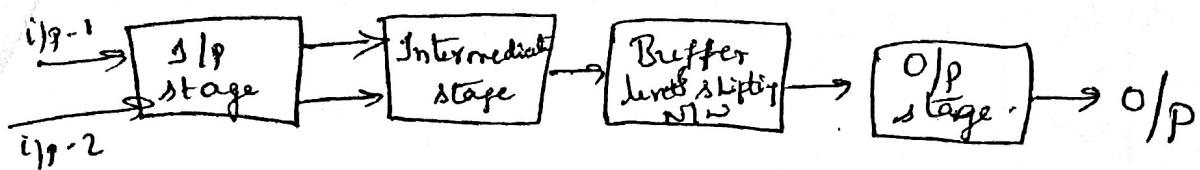

* IIP stage:- The 1st stage is a dual i/p balanced differential amplifier used for providing very high gain of the order 60dB, in order to increase CMRR & i/p impedance of an Op-amp.

* Intermediate stage:- This stage is a dual i/p unbalanced diff amplifier which is driven by the o/p of the first stage.

This stage provides the half the gain provided by the first stage & has two i/p terminals, single o/p terminal so this type of amplifier is called as unbalanced amplifier.

Level shifting stage:- It is usually an emitter follower Ckt used to shift the dc level at the o/p of the intermediate stage of the op-amp to zero volt w.r.t gnd.


This stage amplifies both ac as well as dc signals.

due to absence of capacitance coupling, hence a small amount of dc component will be present at the o/p of the first stage & this dc component will be amplified by stage 3 & drives the transistors into saturation. This causes the o/p wif to be distorted & dc shift will be present. In order to reduce distortion & dc shift we use level shifter in the third stage.

The basic requirements of an o/p stage are low impedance, large

(b4) O/p stage:- AC o/p voltage swing & high current sourcing & sinking capability. The push-pull complementary amplifier meets all these requirements & hence used as the voltage swing is symmetrical w.r.t. gnd.





* Closed loop Configuration of Op-Amp:-

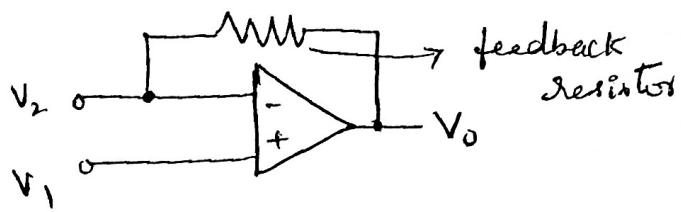

* The advantages of -ve fb are

- It reduces the gain & makes it controllable.
- It — the possibility of distortion
- It ↑ the B.W
- It ↑ the R_i
- It ↓ the R_o

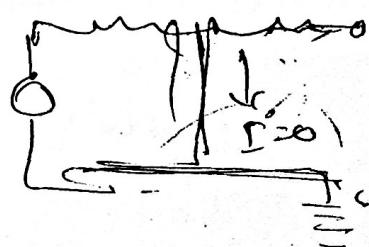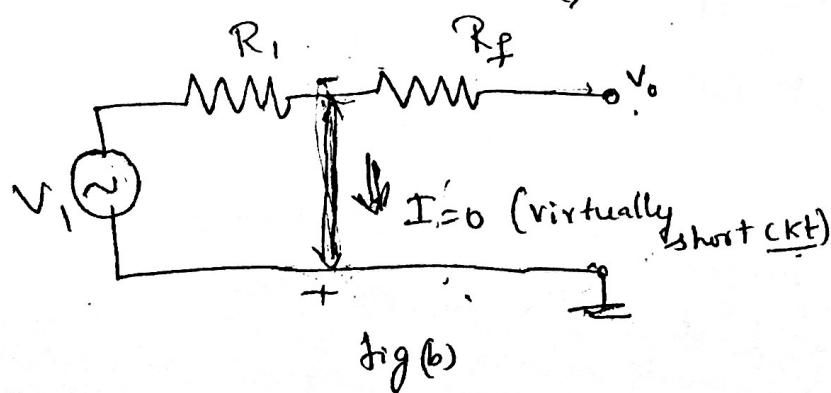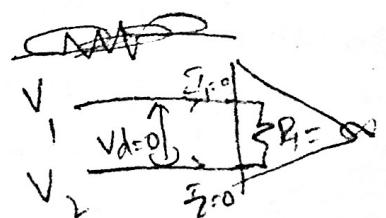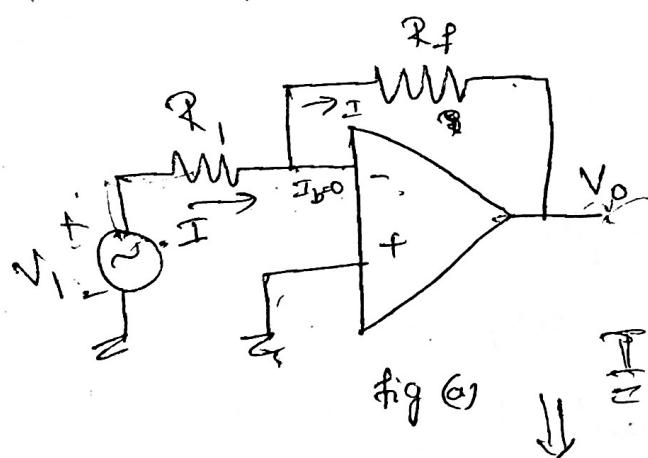* Concept of Virtual short in an Op-Amp :-



N.K.t differential o/p voltage at o/p terminal of Op-Amp is essentially zero.

Since open loop gain of Op-Amp is very large & even for a small o/p voltage the op-amp difference o/p voltage is approximately zero.

$$\begin{aligned} V_o &= 10^4 V_{d2} \quad \therefore A_{O2} = \frac{V_o}{V_d} \\ A_{O2} &= 10^4 \quad \therefore V_d = \frac{V_o}{A_{O2}} \\ \therefore V_d &= \frac{V_o}{10^4} \quad \text{or} \quad V_d = \frac{V_p}{A_{O2}} \end{aligned}$$

$$\text{But } V_d = V_2 - V_1$$

$$(V_2 - V_1) = V_p - V_2$$

$$\therefore V_2 - V_1 = \frac{V_o}{A_{O2}}$$

When $A_{O2} \rightarrow \infty$, (~~open~~) $V_d \rightarrow 0$

$$\therefore (V_2 - V_1) = \frac{V_p}{\infty} = 0$$

$$\frac{1}{\infty}$$

$$\begin{aligned} A_{O2} &= \infty \\ A_{O2} &= \frac{V_o}{V_d} \\ A_{O2} &= \frac{V_o}{V_d} \\ V_o &= A_{O2} V_d \\ V_d &= \frac{V_o}{A_{O2}} \\ \therefore V_d &= \frac{V_o}{\infty} = 0 \end{aligned}$$

\therefore voltage at inverting terminal $V_2 = V_1$ voltage at non-inverting terminal.

From Eqn (3) the voltage at inverting terminal is always equal to the voltage at the non-inverting terminal.

Hence both the i/p terminals are virtually shorted as shown in the fig(b), but no current flows through the virtually shorted ckt branch i.e., there is no physical connection b/w inverting & non-inverting i/p terminals which is called virtual ground concept.

- * From fig(b) the non-inverting terminal is directly connected to ground due to virtual ground concept the voltage at inverting terminal is also equal to zero.
- * When open loop gain of the op-amp is very large & the o/p of the op-amp is very low, then we say that the potential at inverting terminal i/p is equal to potential at non-inverting i/p & there exists a short called virtual short.

Real short

- * Current flows b/w two p/t which are really shorted

- virtual short

- * Current cannot flow b/w two p/t which are ~~really~~ virtually shorted.

Op-Amp Applications :-

Applications are classified as

- linear
- Non-linear

* linear Application:- In this type the o/p voltage of

an Op-Amp varies linearly with r.t. i/p voltage.

* The ω -re fb is the base of linear applications.

Examples:- voltage follower, diff amplifier, Inverting

& non-inverting amplifiers etc

* Non-linear applications:-


A fb is provided from o/p terminal to

either inverting i/p or non-inverting i/p terminal using

non-linear elements like diode, transistors etc.

Examples:- Comparators, Clamper, limiters etc.

* Inverting Amplifier :-

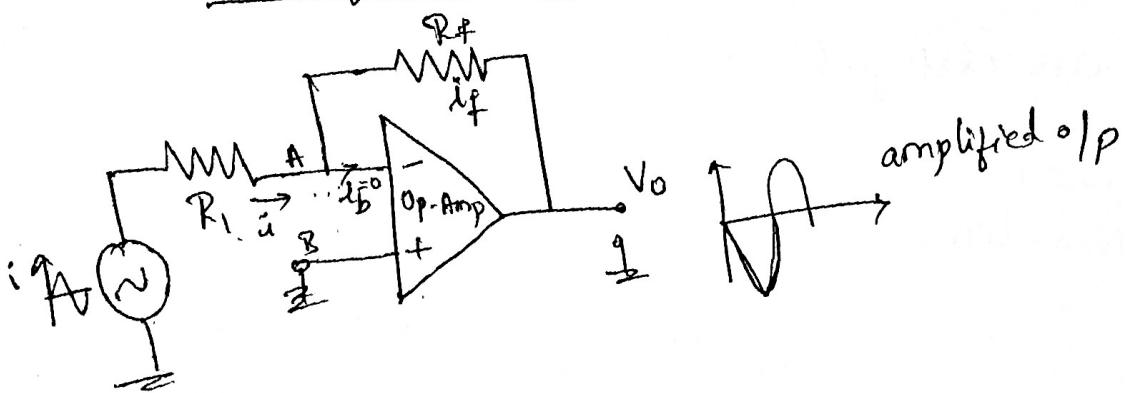

But
then

* An inverting amplifier is a closed loop amplifier in which the i/p is applied to the inverting terminal i/p.

* The o/p of the amplifier is out of phase by 180° w.r.t the i/p.

Now applying KCL at the node 'A' we get,

$$i = i_b + i_f \quad \text{--- (1)}$$

here $i_b = 0$ \because ideal op-amp has an ∞R_i
& hence current drawn will be zero.

$$\therefore i = i_f \quad \text{--- (2)}$$

Apply Ohm's law to find currents i & i_f we get

$$\frac{V_i - V_A}{R_1} = \frac{V_A - V_O}{R_f} \quad \text{--- (3)}$$

But $V_A = V_B = 0 \therefore$ from virtual concept

then Eqn (3) becomes,

$$\frac{V_i}{R_1} = \frac{-V_o}{R_f} \quad - \quad (4)$$

$$\frac{V_o}{V_i} = \frac{-R_f}{R_1}$$

The factor $\frac{V_o}{V_i}$ is called closed loop gain A_F

$$\therefore A_F = \frac{-R_f}{R_1}$$

- sign means that the closed loop amplifier provides phase shift of 180° from cip to oip.


$$\therefore V_o = \frac{-R_f}{R_1} V_i$$

$$\text{or } \underline{V_o = A_F V_i}$$

* Here the closed loop gain is the ratio of two resistors $R_f & R_1$.

This means the gain can be changed by changing the values of $R_f & R_1$,

* Voltage follower :-

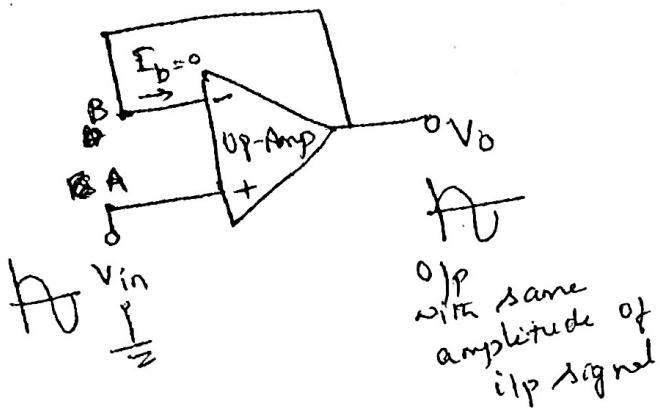

* In an amplifier, if the o/p voltage is equal to the i/p voltage it is called voltage follower (or), unity gain amplifier (or) emitter follower.

* From the Ckt, the i/p is applied at non-inverting i/p of the op-amp.

The o/p of the amplifier & the inverting i/p is shorted \therefore from the Ckt the voltage from 'A' is equal to o/p voltage V_o .

$$\therefore V_A = V_o \quad \text{--- (1)}$$

But $i_B = 0$

$$\therefore V_i = V_B \quad \text{--- (2)}$$

$$\therefore V_A = V_B \quad \text{--- (3)}$$

From (1) & (2)

$$V_o = V_i$$

This Ckt is called as voltage follower because the o/p voltage is equal to & in phase with i/p voltage.

\therefore The voltage gain is given by,


$$A_v = \frac{V_o}{V_i} = \frac{A}{A+1} \quad \text{where } A \gg 1$$

neglecting unity in the eqns

$$A_v = \frac{V_o}{V_i} = \frac{A}{A} = 1$$

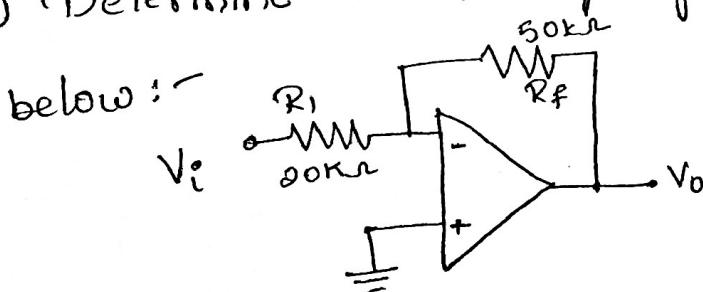Problems:-

① Determine the voltage gain of the Op-Amp Ckt shown below:-



Soln:-


$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_i} = -\frac{50K}{20K} = -\underline{\underline{2.5}}$$

Gain in dB = $A_v (\text{dB})$

$$= 20 \log (A_v)$$

$$= 20 \log (2.5) = \underline{\underline{7.95 \text{dB}}}$$

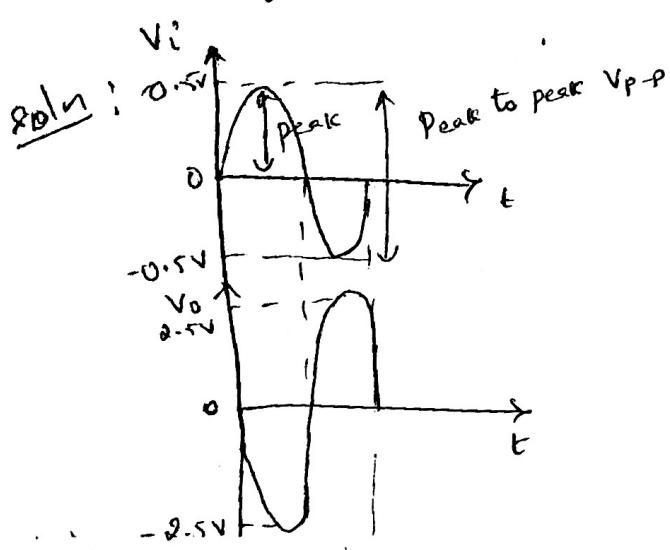2) A sine wave of 0.5 peak voltage is applied to an inverting amplifier using $R_i = 10\text{ k}\Omega$ & $R_f = 50\text{ k}\Omega$. If the supply voltage of $\pm 12\text{ V}$. Determine the O/P voltage & sketch the w/f. If now the amplitude of i/p sine wave is increased to 5V what will be the O/P? Is it practically possible? sketch the waveform.



$$A_v(\text{dB}) = \frac{-R_f}{R_i} = \frac{-50\text{ k}}{10\text{ k}} = -5$$

when $V_i = 0.5\text{ V}$ (peak)

$$\therefore \frac{V_o}{0.5} = -5$$


$$\therefore V_o = -0.5 \times 5 = -2.5\text{ (peak)}$$

when $V_i = 5\text{ V}$, then

$$A_v = \frac{V_o}{V_i} = -5$$

$$\frac{V_o}{5} = -5$$

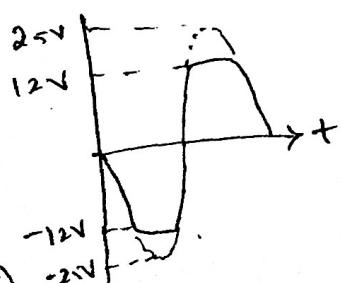
$$\therefore V_o = -5 \times 5 = -25\text{ V (peak)}$$



$V_o = A_d(V_2 - V_1)$

V_o o/p don't
is limited to $\pm 12\text{ V}$
it is limited by power supply

Inverting Summer or Adder

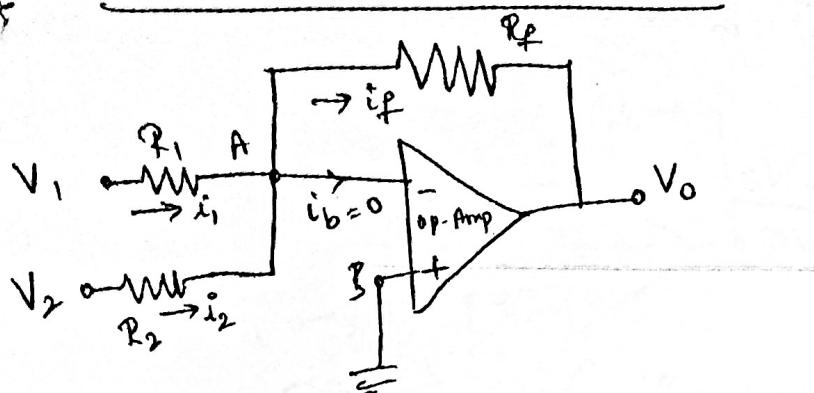

* If two or more i/p signals are applied to inverting terminal of Op-Amp, the o/p is sum of these i/p's this is called inverting Summer.

* Let V_1 & V_2 be the i/p voltages applied to inverting i/p of an Op-amp through R_1 & R_2 .

* The f/b resistor R_f connected b/n o/p to inverting i/p of Op-Amp & non-inverting i/p terminal is grd.

Now applying KCL at node 'A' we get,

$$i_1 + i_2 = i_f + i_b \quad \text{--- (1)}$$

But $i_b = 0$

$$\therefore i_1 + i_2 = i_f \quad \text{--- (2)}$$

Now applying Ohm's law to find Current

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} = \frac{V_A - V_0}{R_f} \quad \text{--- (3)}$$

According to virtual ground concept $V_A = V_B = 0$

\therefore Eqn (3) becomes

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{-V_0}{R_f}$$

$$V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \quad \text{--- (4)}$$

Let us substitute $R_1 = R_2 = R_f = R$ in Eqn (4)


$$\therefore V_0 = -\frac{R}{R} (V_1 + V_2)$$

$$\underline{\underline{V_0 = -(V_1 + V_2)}}$$

* Therefore the o/p of Op-amp is equal to sum of two c/p voltages.

* The -ve sign indicates that o/p voltage is 180° out of phase w.r.t. to the c/p voltage.

Subtractor or Difference Amplifier :-

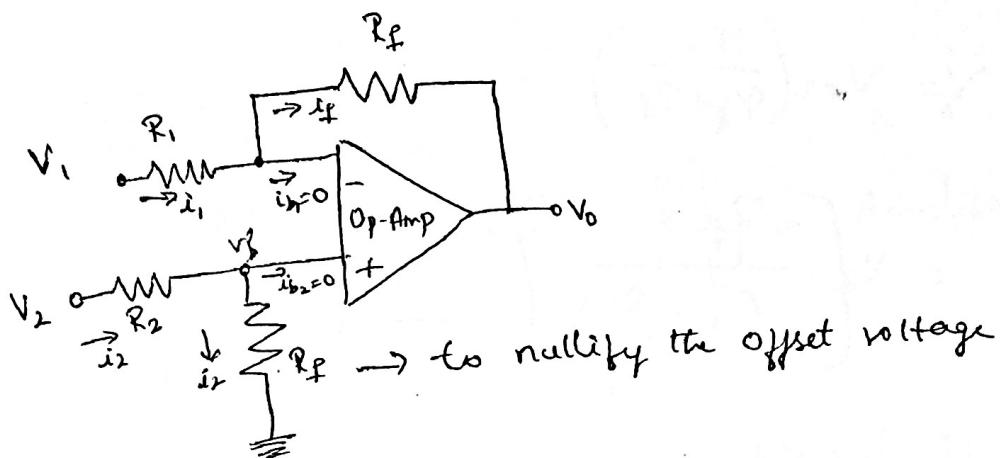


* The subtractor ckt consists of two sig & is given to inverting & non-inverting terminal of the Op-Amp.

Let us obtain the V_0 using superposition principle by applying the following steps:-


step 1 :- Reduce V_2 to zero & find the o/p v/tg due to V_1 :-
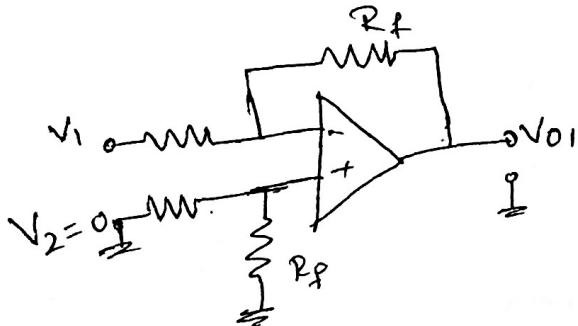
$$V_{O1} = -\left(\frac{R_f}{R_1}\right) V_1 \quad \text{--- (1)}$$



step 2 :- Reduce V_1 to zero & find the o/p v/tg due to V_2 :-
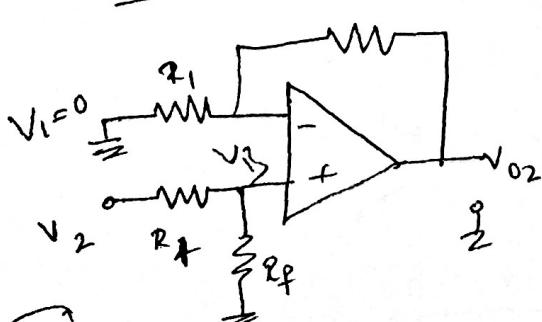
$$V_{O2} = \left(1 + \frac{R_f}{R_2}\right) V_2 \quad \text{--- (2)}$$



where ' V_B ' is the voltage drop across R_f .

$$\therefore V_B = V_{02} \left(\frac{R_f}{R_1 + R_f} \right)$$

$$= V_2 \left[\frac{R_f}{R_1 \left(1 + \frac{R_f}{R_1} \right)} \right] - \textcircled{3}$$

Substituting Eqn $\textcircled{3}$ into $\textcircled{2}$ we get

$$V_{02} = V_2 \left(\frac{R_f}{R_1} \right) - \textcircled{4}$$

Step 3:- Resulting opv V_0 is given by principle of superposition

$$\therefore V_0 = V_{01} + V_{02}$$

$$= -\left(\frac{R_f}{R_1}\right)V_1 + \left(\frac{R_f}{R_1}\right)V_2$$


$$V_0 = \frac{R_f}{R_1} (V_2 - V_1) - \textcircled{5}$$

If we choose $R_f = R_1$, then

$$V_0 = V_2 - V_1 - \textcircled{6}$$

Hence the given CCT works as subtractor.

Non-Inverting Amplifier :-

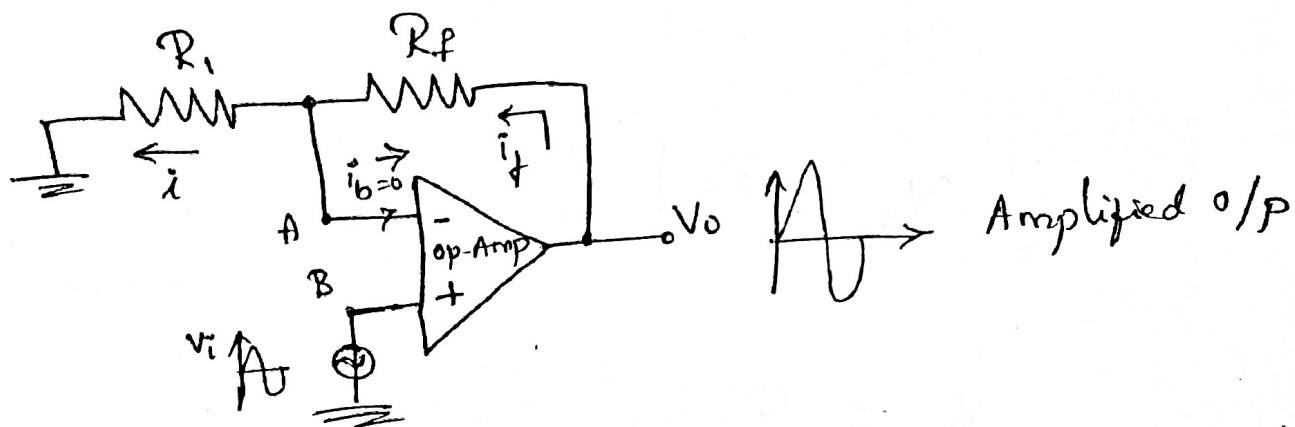

* In this amplifier circuit, the i/p signal is amplified without producing any phase shift b/w i/p & o/p signals. Hence it is called as non-inverting amplifier.

Now apply KCL at the node 'A' we get,

$$i_f = i_b + i \quad \text{--- (1)}$$

$i_b = 0$ Since ideal op-Amp draws zero current

$$\therefore i_f = i \quad \text{--- (2)}$$

Apply Ohm's law to find current i_f & i

we get,

$$\frac{V_o - V_A}{R_f} = \frac{V_A - 0}{R_1} \quad \text{--- (3)}$$

Since $V_A = V_B = V_{in}$

\therefore Eqn (3) is modified as

$$\frac{V_o - V_{in}}{R_f} = \frac{V_{in}}{R_1} \quad \text{--- (4)}$$

$$\therefore \frac{V_o}{R_f} = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_f}$$

$$V_o = R_f \left[\frac{V_{in}}{R_1} + \frac{V_{in}}{R_f} \right].$$

$$V_o = R_f V_{in} \left[\frac{R_f + R_1}{R_1 R_f} \right]$$

$$\frac{V_o}{V_{in}} = \frac{R_f + R_1}{R_1}$$


$$\frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_1}$$

$$\therefore \underline{\underline{V_o = V_{in} \left(1 + \frac{R_f}{R_1} \right)}}$$

$$\underline{\underline{A_f = \left(1 + \frac{R_f}{R_1} \right)}}$$

$$\therefore \underline{\underline{V_o = V_{in} A_f}}$$

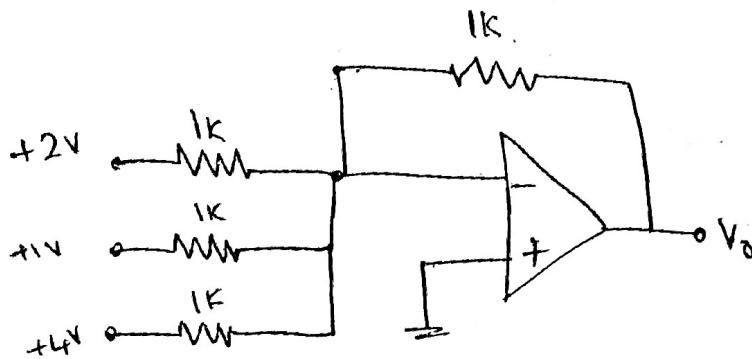Q) Determine the O/p voltage for the Op-Amp adder Ckt shown



Soln :-

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$= - [V_1 + V_2 + V_3]$$

$$\underline{\underline{V_o = -7V}}$$

② Design a scaling adder Ckt using Op-Amp to give the

$$\text{O/p } V_o = - (8V_1 + 6V_2 + 5V_3)$$

Soln :-


$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$\text{Let } R_f = 100\text{ k}\Omega$$


$$\text{Given } \frac{R_f}{R_1} = 8, R_1 = \frac{R_f}{8} = \frac{100}{8} = 12.5\text{ k}\Omega$$

$$\frac{R_f}{R_2} = 6, R_2 = 16.66\text{ k}\Omega$$
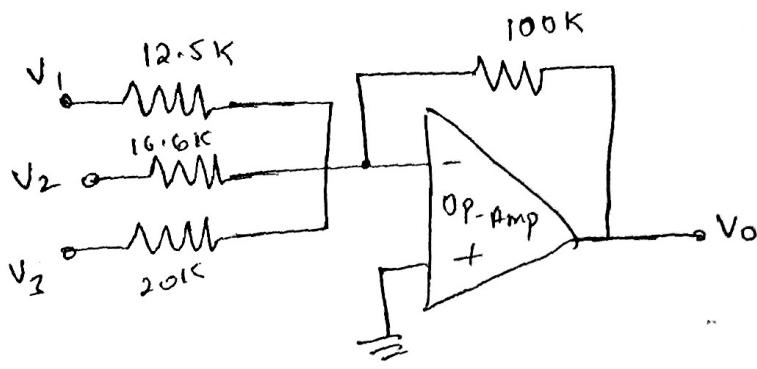
$$\frac{R_f}{R_3} = 5, R_3 = 20\text{ k}\Omega$$



* Integrator :-

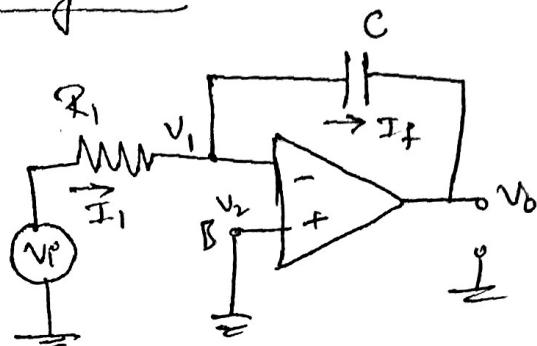

The op voltages are proportional to the input voltage integrated over time.

* An integrator Ckt can be designed using only passive elements (R, L, C) such an integrator is called passive integrator.

* It has a capacitor in the fb loop.

* Since non-inverting i/p terminal is grounded $\therefore V_2 = 0$
Due to virtual gnd $V_1 = V_2 = 0$

* Due to high i/p impedance of op-amp the flow of current into its inverting terminal is zero. \therefore Same current flows through R & C

$$\therefore I_1 = I_f = \text{constant} \quad \text{--- (1)}$$

$$\text{But } I_1 = \frac{V_{i0} - V_i}{R} = \frac{V_i}{R} \quad \text{--- (2)}$$

$$\& I_f = C \frac{d}{dt} [V_i - V_o]$$

$$I_f = -C \frac{dV_o}{dt} \quad \text{--- (3)}$$

Substituting (2) & (3) into (1) we get

$$\frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_i$$

Integrating both sides w.r.t t' we have

$$V_o = -\frac{1}{RC} \int_0^t V_i dt + V_o(0) \quad \text{--- (4)}$$

where $V_o(0)$ is the initial voltage on the capacitor at

$$t=0$$

* From Eqn (4) we find that the o/p V_o is proportional to the integral of the i/p V_i .

If the initial V_o on the capacitor at $t=0$ is zero

$$\text{then } V_o(0) = 0$$


$$\therefore V_o = -\frac{1}{RC} \int_0^t V_i dt$$

* The O/p of integrator is a cosine w/r if an i/p sinusoidal.

* If the i/p is step type , o/p is ramp type

* ————— square type o/p is triangular wave.

* Differentiator :-

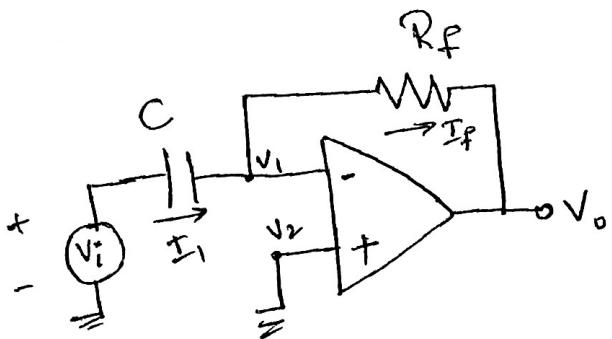

The O/P of the Ckt is approximately directly proportional to the rate of change of the i/p.

* The Ckt of op-amp differentiator can be obtained

from op-amp integrator Ckt by simply interchanging the position of R & C.

* Since $V_2 = 0$ due to virtual ground concept.

$$\therefore V_1 = V_2 = 0.$$

* Due to high impedance of op-amp current flow through R & C is

$$I_1 = I_f \quad \text{--- (1)}$$

$$\text{But } I_i = C \frac{d}{dt} [V_i - V_0]$$

$$= C \frac{dV_i}{dt} - \textcircled{2}$$

$$\& T_f = \frac{V_i - V_0}{R}$$

$$= -\frac{V_0}{R} - \textcircled{3}$$

Using these Eqns in ① we get

$$C \frac{dV_i}{dt} = -\frac{V_0}{R}$$

$$\therefore V_0 = \underline{-RC \frac{dV_i}{dt}}$$

* If i/p is step type o/p is spike

* If i/p is sine type o/p is cosine w/f.

* Signal conversion using Op-Amp :-

(1) Integrator :-

Consider time constant $R_C = 1$ & initial o/p voltage

$$V_o(0) = 0V$$

\rightarrow Step i/p :-

A step i/p signal with a magnitude of 'A' volts applied at the i/p & it is expressed as,

$$V_{in}(t) = A \quad \text{for } t \geq 0$$


$$V_{in}(t) = 0 \quad \text{for } t < 0$$

$$\therefore V_o(t) = - \int_0^t V_{in}(t) dt$$

$$= - \int_0^t A dt$$

$$= -A \int_0^t dt$$

$$V_o(t) = -A [t]_0^t$$

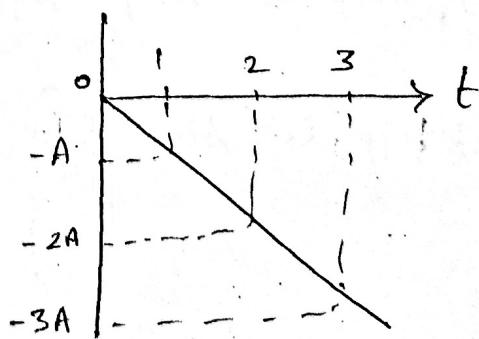

* The o/p voltage tends to max at 't' $\rightarrow \infty$