

**BCD Adder, Binary Multiplier,  
Multiplexers, De-Multiplexers,  
Decoders, Encoders, Parity  
Circuits and Comparators**

## BCD Adder

### The Rules for BCD addition:

- 1) When the BCD sum is less than or equal to 1001 without a carry, the corresponding BCD digit is correct. No correction needed.
- 2) When the BCD sum is greater than 1001, without a carry, the result is invalid. The addition of binary 6 (0110)<sub>2</sub> to the sum converts it to the correct digit.
- 3) When the BCD sum is less than or equal to 1001, but with a carry '1', the result is again invalid. The addition of binary 6 (0110)<sub>2</sub> to the sum converts it to the correct digit.


Example: Perform BCD addition of 448 + 489.

Soln:

$$\begin{array}{r}
 \begin{array}{r}
 \begin{array}{r}
 11 \\
 448 \\
 + 489 \\
 \hline
 937
 \end{array} \\
 \end{array}
 \quad
 \begin{array}{r}
 \begin{array}{r}
 1 \quad 1 \quad 1 \\
 0100 \quad 0100 \quad 1000 \\
 + 0100 \quad 1000 \quad 1001 \\
 \hline
 1001 \quad 1101 \quad 0001 \\
 \hline
 1001 \quad 0011 \quad 0111
 \end{array} \\
 \begin{array}{l}
 \text{Rule 1} \quad \text{Rule 2} \quad \text{Rule 3}
 \end{array}
 \end{array}
 \end{array}$$

P.T.O

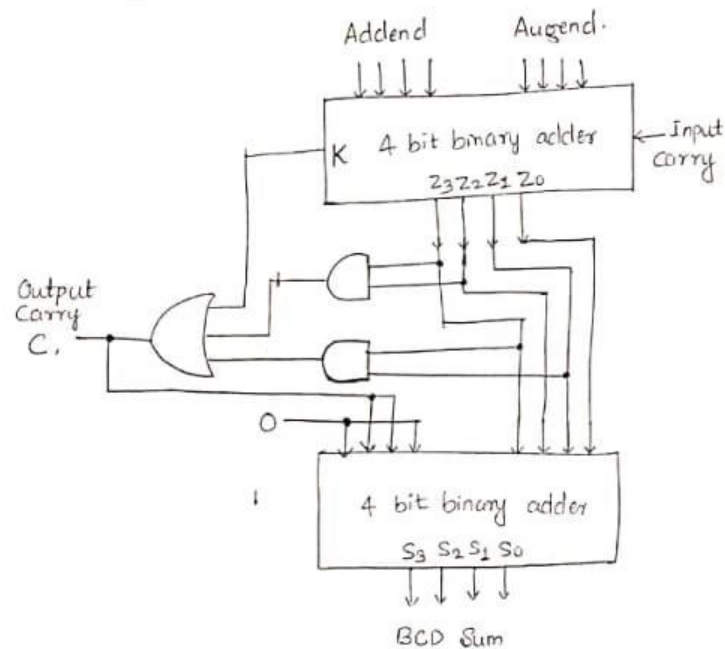A BCD adder that adds two BCD digits and produces a sum digit in BCD is shown below.



Block Diagram of BCD Adder

It has two 4-bit binary adders and correction logic. The two decimal digits, together with an input carry, are added in the first 4-bit binary adder, to produce the binary sum.

The condition for correction can be expressed by the boolean function  $C = K + Z_3 Z_1 + Z_3 Z_2$ .

Here 'C' is the output carry from the BCD adder, & 'K' is the output carry from the first binary adder. The two terms with the 'Z' variables detect the binary outputs from 1010 through 1111.

P.T.O

When the BCD carry is equal to '0', '0000' is added to the binary sum. This condition occurs if the sum of two BCD numbers and carry is less than or equal to 1001.

When the BCD carry is equal to '1', '0110' is added to the binary sum through the second 4-bit binary adder. This condition occurs when the sum of BCD is greater than 1001 without carry and also for when BCD sum is less or equal to 1001 without carry.

### BINARY MULTIPLIERS.

Multiplication of binary numbers is performed in the same way as with decimal numbers.

The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit.

Each such multiplication forms a partial product.


Successive partial products are shifted one bit to the left.

The final product is obtained from the sum of the partial products.

To see how a binary multiplier can be implemented with a combinational circuit, consider the multiplication of two 2-bit numbers, as shown below.

The multiplicand bits are  $B_1$  &  $B_0$ , the multiplier bits are  $A_1$  &  $A_0$ , and the product is  $P_3 P_2 P_1 P_0$ .
 
$$\begin{array}{r}
 \begin{array}{cc} B_1 & B_0 \\ A_1 & A_0 \end{array} \\
 \hline
 \begin{array}{ccc} A_0 B_1 & A_0 B_0 & \\ A_1 B_1 & A_1 B_0 & + \end{array} \\
 \hline
 \begin{array}{cccc} P_3 & P_2 & P_1 & P_0 \end{array}
 \end{array}$$



A 2x2 Binary Multiplier

The first partial product is formed by multiplying  $B_1 B_0$  by  $A_0$ .

The multiplication of two bits such as  $A_0$  and  $B_0$  produces '1' if both bits are '1', otherwise it produces a '0'. This is identical to an AND operation. Therefore, the partial product can be implemented with AND gates as shown above.

The second partial product is formed by multiplying  $B_1 B_0$  by  $A_1$ , and is shifted one position to the left. The two partial products are added with two half adder (HA) circuits.

Note that the least significant of the product does not have to go through an adder, since it is formed by the output of 1st AND gate.

A combinational circuit binary multiplier with more bits can be constructed in a similar fashion.

A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in multiplier.

The binary o/p in each level of AND gates is added in parallel with the partial product of the previous level to form a new partial product. The last level produces the product.

For  $M$  multiplier bits and  $N$  multiplicand bits, we need  $M \times N$  AND gates

$(M-1)$ ,  $N$  bit adders to produce a product of  $M+N$  bits.


for example: Let Multiplicand is  $B_3 B_2 B_1 B_0$  &  
Multiplier is  $A_2 A_1 A_0$

Since  $M=3$  &  $N=4$ , we need  $3 \times 4 = 12$  AND gates

$(3-1)$  4 bit Adders

= 2, 4-bit Adders to produce a product

of  $3+4 = 7$  bits.

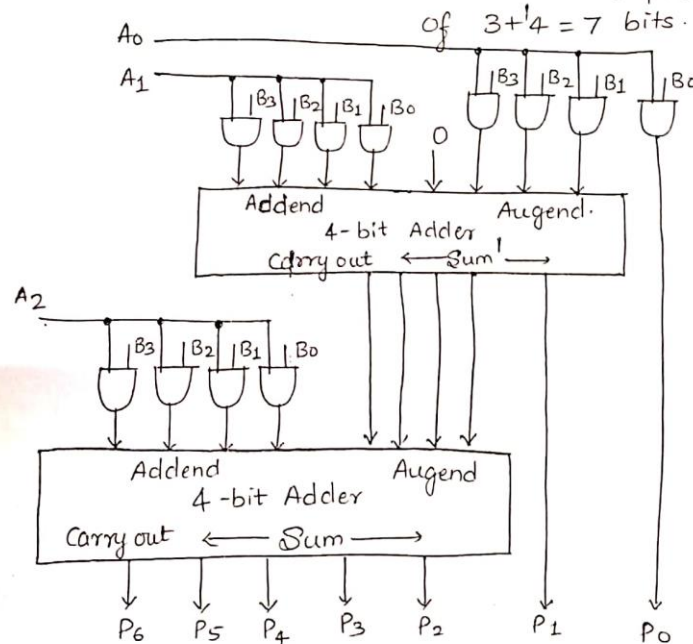

A 4x3 bit Binary Multiplier



# MULTIPLEXERS (MUX)


Multi Inputs : Single Output

A multiplexer is a combinational circuit that selects binary information from one of many input lines and sends the information to a single output line.


The selection of a particular input line is controlled by a set of input variables, called Selection inputs.

Normally, there are  $2^n$  input lines and  $n$  selection inputs whose bit combinations determine which input is selected. ( $2^n:1$  is the MUX configuration).

↑  
inputs    ↑  
          output

 

 A simple 2:1 MUX is as shown below ( $2:1 = 2^1:1$ )



Truth Table

S	d0	d1	f
0	1	0	d0
1	0	1	d1

OR

S	y
0	d0
1	d1

$\therefore n=1$   
select line

Note: In Mux any one input bit will be high at an instant of time.


From the truth table, it is seen that

if  $S=0$ ,  $d_0$  input is selected and sent to the o/p.


$S=1$ ,  $d_1$  input is selected and sent to the o/p

$$\therefore Y = \bar{S}d_0 + Sd_1$$

Realization of 2:1 Mux using gates →

 


4:1 MUX ( $2^2:1$ ,  $n=2$ )

 

S1	S0	y
0	0	d0
0	1	d1
1	0	d2
1	1	d3

 
$$\therefore Y = \bar{S}_1\bar{S}_0d_0 + \bar{S}_1S_0d_1 + S_1\bar{S}_0d_2 + S_1S_0d_3$$



Realization of 4:1 MUX using gates

4:1 MUX  
Circuit diagram

8:1 MUX ( $2^3:1$ ,  $n=3$ )

 


S2	S1	S0	y
0	0	0	d0
0	0	1	d1
0	1	0	d2
0	1	1	d3
1	0	0	d4
1	0	1	d5
1	1	0	d6
1	1	1	d7

$$\therefore Y = \bar{S}_2\bar{S}_1\bar{S}_0d_0 + \bar{S}_2\bar{S}_1S_0d_1 + \bar{S}_2S_1\bar{S}_0d_2 + \bar{S}_2S_1S_0d_3 + S_2\bar{S}_1\bar{S}_0d_4 + S_2\bar{S}_1S_0d_5 + S_2S_1\bar{S}_0d_6 + S_2S_1S_0d_7$$

Exercise 1: Configure 4:1 MUX using 2:1 MUX.


Sol<sup>n</sup>

 

Let us say address or select lines  $S_1S_0 = 10$  then  
for  $S_1 = 1$  places  $x_1$  at  $d_1$  &  $x_3$  at  $d_1$   
for  $S_0 = 0$  places  $x_1$  at the final output.

Exercise: Configure 16:1 MUX using 4:1 MUX.

Sol<sup>n</sup>

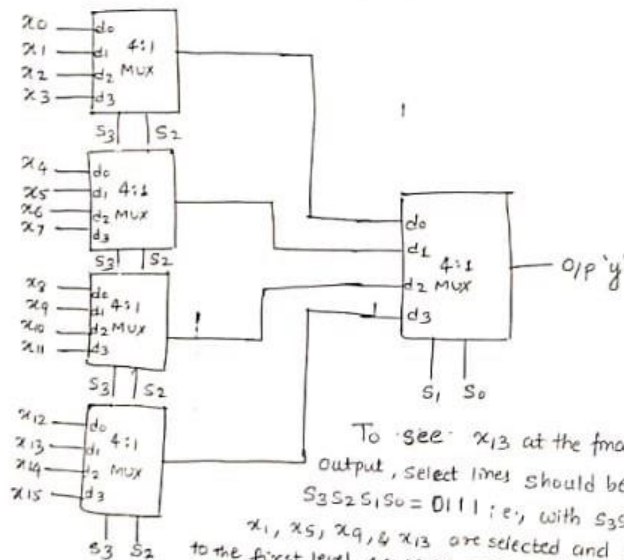


To see  $x_{13}$  at the final output, select lines should be  $S_3S_2S_1S_0 = 0111$  i.e., with  $S_3S_2 = 01$   $x_1, x_5, x_9$  &  $x_{13}$  are selected and sent to the first level 4:1 MUX o/p's & these acts like i/p's to second level 4:1 MUX,  $S_1S_0 = 11$ ,  $x_{13}$  is selected at  $y$ .

Exercise: Implement the following function using 8:1 MUX

 Q.12

$$f(a, b, c) = \sum m(0, 4, 5, 6)$$

Let  $d_0 = d_4 = d_5 = d_6 = 1$  &  
 $d_1 = d_2 = d_3 = d_7 = 0$  in a 8:1 MUX



Exercise: Implement the following function using 4:1 MUX

$$f(a, b, c) = \sum m(0, 1, 2, 7)$$

Sol<sup>n</sup>. The given function is 3 variable function i.e., we get 8 combination of 3 variables. So it can be directly implemented using 8:1 MUX as we did in previous example. But asked is to implement using 4:1 MUX. So we have to minimize the given function.

The algebraic form of given function is

$$\begin{aligned} f(a, b, c) &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + abc \\ &= \bar{a}\bar{b}(\bar{c} + c) + \bar{a}b\bar{c} + abc \end{aligned}$$

$$f(a, b, c) = \bar{a}\bar{b}(1) + \bar{a}b\bar{c} + abc$$

$$f(a, b, c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + abc$$


Let's compare this eqn with 4:1 MUX general equation

$$f = \bar{S}_1\bar{S}_0(d_0) + \bar{S}_1S_0(d_1) + S_1\bar{S}_0(d_2) + S_1S_0(d_3)$$

Here  $a$  &  $b$  will be acting as select lines & ' $c$ ' will be the data lines


$$d_0 = 1, d_1 = \bar{c}, d_2 = 0, d_3 = c$$

 as we don't have  $\bar{a}\bar{b}$  combination in the simplified equation for  $d_2$



 Exercise: Implement  $f(a, b, c) = \Sigma m(1, 4, 5, 7)$  using 4:1 MUX using ' $b$ ' and ' $c$ ' as select lines


$$\text{Sol}^n: f(a, b, c) = \Sigma m(1, 4, 5, 7)$$



- $b=0, c=0$  corresponds to cells 0 & 4
- $b=0, c=1$  corresponds to cells 1 & 5
- $b=1, c=0$  corresponds to cells 2 & 6
- $b=1, c=1$  corresponds to cells 3 & 7


P.T.O.

Filling the function values we have

 

$d_0$ -map


$$d_0 = a$$

 

$d_1$ -map


$$d_1 = \bar{a} + a$$

$$d_1 = 1$$

 

$d_2$ -map


$$d_2 = a$$

 

$d_3$ -map

$$d_3 = 0$$

 
Here ' $a$ ' is acting as data line & ( $b, c$ ) acting as Select lines.  $\therefore d_0, d_1, d_2, d_3$  takes values only in terms of ' $a$ '.



Example: Implement the following function using 8:1 MUX. Treat  $a, b$  &  $c$  as select lines.

$$f(a, b, c, d) = \Sigma m(0, 1, 5, 6, 7, 9, 10, 15)$$

Sol<sup>n</sup>:

 


P.T.O.



From the map.
 
$$d_0 = 1, d_1 = 0, d_2 = d, d_3 = 1, d_4 = d, d_5 = \bar{d}, d_6 = 0, d_7 = d$$



Exercise: Implement  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 9, 10, 15)$  using 4:1 MUX with  $a$  &  $b$  as select lines.

Sol<sup>n</sup>




$$d_0 \text{ map} \therefore d_0 = \bar{c}$$


$$d_1 \text{ map} \therefore d_1 = c + d$$


$$d_3 \text{ map} \therefore d_3 = cd$$


$$d_2 \text{ map} \therefore d_2 = \bar{c}d + c\bar{d} = c \oplus d$$

P.T.O.

 

Exercise: Implement the boolean function

$f(a, b, c, d) = \sum m(0, 2, 4, 5, 7, 9, 10, 14)$  using Multiplexers with two 4:1 MUX with variables  $(a, d)$  connected to their select lines in the first level. And one 2:1 MUX with variable 'c' connected to its select line in the second level.

$$\text{Sol<sup>n</sup>: } f(a, b, c, d) = \sum m(0, 2, 4, 5, 7, 9, 10, 14)$$


$$\leftarrow c=0 \rightarrow \leftarrow c=1 \rightarrow$$

Such problems can be solved in simpler way.

Divide the whole K-map with single variable acting as select line in the problem definition.

P.T.O.




From problem definition, variable 'c' is acting as a select line of 2:1 MUX in second level.

$C = 0$  &  $C = 1$  if its a select line for 2:1 MUX

∴ Look into the K-map wherever we have  $C = 0$  &  $C = 1$   
So when we divide K-map, we get as shown above.

 Let us consider the  $C = 0$  map for final 2:1 MUX



( $a=0, d=0$ ) represents  $d_0$

( $a=0, d=1$ ) represents  $d_1$

( $a=1, d=0$ ) represents  $d_2$

( $a=1, d=1$ ) represents  $d_3$


Here  $a$  &  $d$  are select lines  
of 4:1 MUX in first level.

Let us write  $d_0, d_1, d_2, d_3$  in terms of 'b'

$$d_0 = 1, d_1 = b, d_2 = 0, d_3 = \bar{b}$$

These will be the i/p's of first 4:1 MUX in first level.

Now Let us look at  $C = 1$  map.

 


$$\therefore d_0 = \bar{b} \\ d_1 = b \\ d_2 = 1 \\ d_3 = 0$$

These will be the i/p's  
of second 4:1 MUX  
in first level.

P.T.O

∴ The implementation is shown below.

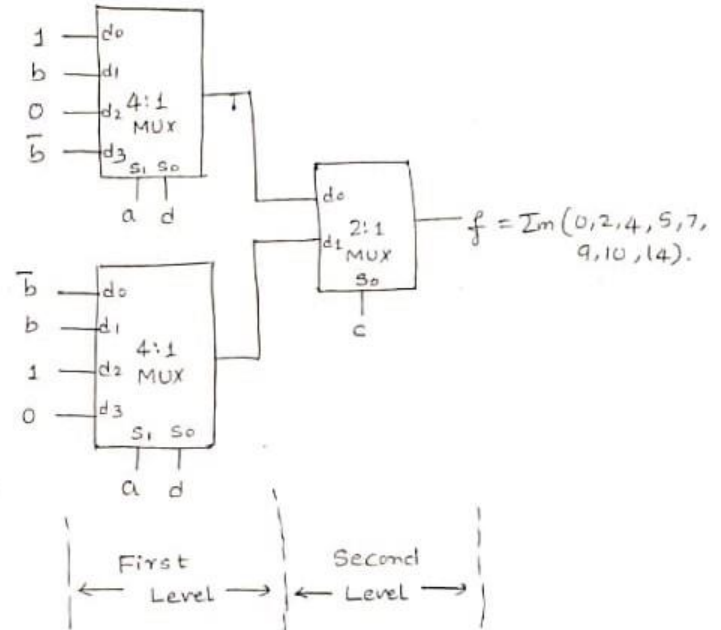

## DEMULTIPLEXERS (DeMUX)


A demultiplexer is a digital function that performs the inverse of the multiplexer operation. i.e., a demultiplexer receives information from a single line and transmits it to one of  $2^n$  possible output lines.

The selection of the specific output is controlled by the bit combination of 'n' selection lines.

Single Input : Multi Outputs

P.T.O

### 1:2 DeMUX ( $1:2^1, n=1$ )

 


$S_0$	$Y_0$	$Y_1$
0	D	0
1	0	D

NOTE: In DeMUX any one o/p bit will be high at an instant of time.


From truth table,

 if  $S=0$ , D is sent to  $Y_0$   
 $S=1$ , D is sent to  $Y_1$




Realization of 1:2 Demux using gates

### 1:4 DeMUX ( $1:2^2, n=2$ )

 


$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

 


Realization of 1:4 DeMUX using gates

### 1:8 DeMUX ( $1:2^3, n=3$ )

 

$S_2$	$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$
0	0	0	D	0	0	0	0	0	0	0
0	0	1	0	D	0	0	0	0	0	0
0	1	0	0	0	D	0	0	0	0	0
0	1	1	0	0	0	D	0	0	0	0
1	0	0	0	0	0	0	D	0	0	0
1	0	1	0	0	0	0	0	D	0	0
1	1	0	0	0	0	0	0	0	D	0
1	1	1	0	0	0	0	0	0	0	D

 


Realization of 1:8 DeMUX using gates


## DECODERS

A decoder is a combinational circuit that converts binary information from the 'n' coded i/p's to a maximum of '2<sup>n</sup>' unique o/p's. i.e.,  $n \text{ inputs} = 2^n \text{ output}$   
 $\therefore (n : 2^n)$ .

Multi Input = Multi Output

 


2:4 Decoder ( $2:2^2, n=2$ )

 

Inputs		Outputs			
$a_1$	$a_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 
$$\therefore Y_0 = \bar{a}_1 \bar{a}_0 ; Y_1 = \bar{a}_1 a_0 ; Y_2 = a_1 \bar{a}_0 \text{ \& } Y_3 = a_1 a_0$$




Note: Any one o/p will be high at an instant of time



### 3:8 Decoder ( $3:2^3, n=3$ )

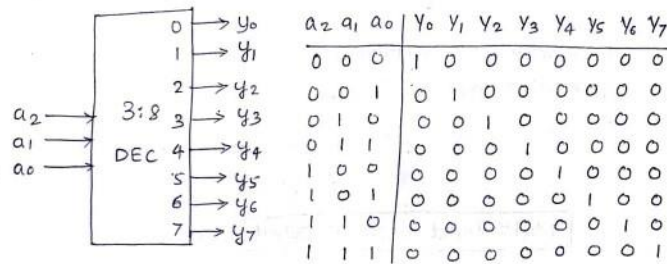

 We can observe here in decoders, that is the i/p is sent to the particular output depending on the value of input.  
for eg: 000 is sent to only  $y_0$ ; 110 is sent to only  $y_6$



### Logic Design Using Decoders

We observe that each o/p of the decoder generates a minterm (i.e., product of i/p combinations)

2:4 DEC generates 4 minterms using two input variables.


3:8 DEC generates 8 minterms using three input variables.

Thus,  $n:2^n$  DEC generates ' $2^n$ ' minterms using ' $n$ ' i/p variables & finally realized a SOP expression.

 Exercise: Implement  $f(a,b,c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + ab\bar{c}$  using 3:8 decoder.


Sol<sup>n</sup>:  $f(a,b,c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + ab\bar{c}$

$$\therefore f(a,b,c) = \sum m(1, 2, 5, 6)$$



Exercise: Implement  $f_1(a,b,c) = \sum m(0, 4, 6, 7)$  &  $f_2(a,b,c) = \sum m(1, 4, 5)$  using 3:8 decoder

Sol<sup>n</sup>

 



Observe that the no. of inputs to each OR-gate would be the no. of minterms in the expression.

We can reduce the no. of i/p's by taking complement of given function (i.e.,  $\bar{f}$ ) instead of  $f$  and finally invert the OR o/p by  $f$ . This can simply be done by replacing the OR gate with a NOR gate.

This can be adopted when the no. of minterms in a function is more than half the total no. of possible minterms.

Exercise: Implement the following functions using a decoder minimizing the no. of i/p's to be summed:

$$f_1(abc) = \sum m(0, 2, 3, 5, 6, 7)$$

$$f_2(abc) = \sum m(1, 3, 4, 6, 7)$$

Sol<sup>n</sup>

$$f_1(abc) = \sum m(0, 2, 3, 5, 6, 7)$$

Here no. of minterms are more than half of the total minterms

$$\therefore \bar{f}_1(abc) = \sum m(1, 4) \text{ in SOP form.}$$

$$\text{OR } f_1(abc) = \text{PIM}(1, 4) \text{ in POS form.}$$

$$\text{Similarly for } f_2(abc) = \sum m(1, 3, 4, 6, 7)$$


$$\bar{f}_2(abc) = \sum m(0, 2, 5) \text{ SOP form.}$$

$$\text{or } f_2(abc) = \text{PIM}(0, 2, 5) \text{ POS form.}$$

We can use any one of the two forms to implement.

P.T.O

The implementation is shown below.

 


Exercise: Implement the following functions expressed in maxterm canonical form using 3 to 8 line decoder minimizing the no. of i/p's.

$$f_1(abc) = \text{PIM}(2, 3, 4, 5, 7)$$

$$f_2(abc) = \text{PIM}(0, 2, 4, 6, 7)$$

Sol<sup>n</sup>: By looking into the expressions, both have its terms more than half of the possible total term.  
 $\therefore$  we take complement of these functions.
 
$$\therefore f_1 = \sum m(0, 1, 6) \text{ \& } f_2 = \sum m(1, 3, 5).$$




Note: for SOP, our goal is to get '1'  
for POS, our goal is to get '0'

In the first example, SOP is converted to POS  $\therefore$  our goal is to get '0', & to get '0' we have to use NOR gate

In the second example, POS is converted to SOP  $\therefore$  our goal is to get '1', to get '1' we have to use OR gate

$\therefore$  In general, we have to concentrate only on the complemented function, if its POS use NOR gate  
if its SOP use OR gate.

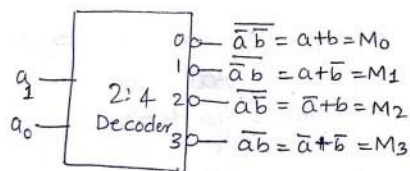Decoders in IC packages usually have an active low output. The truth table and symbol of such 2:4 decoder is shown below.



$\therefore$  These generate maxterms at their outputs and are useful in implementing POS expressions.


Inputs		Outputs			
$a_1$	$a_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	0	0

Exercise: Implement the following functions in maxterm canonical form using 2:4 decoder with active low outputs.

$$f_1(a,b) = \Pi M(1,3)$$

$$f_2(a,b) = \Pi M(0,2,3)$$

Soln

 

Exercise: Implement the following functions using 3:8 decoder with active low outputs.


$$f_1(a,b,c) = \Pi M(0,1,3,5,6)$$

$$f_2(a,b,c) = \Pi M(2,3,4,5,7)$$

Soln

$$f_1(a,b,c) = \Sigma m(2,4,7)$$

$$f_2(a,b,c) = \Sigma m(0,1,6)$$

 

Exercise:  $f_1 = \Pi M(1, 2, 5)$ ,  $f_2 = \Pi M(0, 1, 3, 5, 7)$ .

Implement using 3:8 Dec. with active low o/p's.


Sol<sup>n</sup>:

$f_1$  is having its terms less than the half of its total possible terms.  $\therefore$  No need of complementing.

$f_2$  is having more than half of its total terms  $\therefore$  It has to be complemented.

$$\therefore f_1(abc) = \Pi M(1, 2, 5)$$

$$\bar{f}_2(abc) = \Sigma m(2, 4, 6).$$

 

Exercise:


$$f_1(abc) = \Sigma m(0, 2, 4); f_2(abc) = \Sigma m(1, 2, 4, 5, 7)$$

Implement with uncomplemented o/p's (active high o/p's).

Sol<sup>n</sup>:

$$f_1(abc) = \Sigma m(0, 2, 4)$$

$$f_2(abc) = \Pi M(0, 3, 6).$$

 

Note:

In active high output decoder

Use OR gate to implement SOP form

Use NOR gate to implement POS form

In active low output decoder

Use NAND gate to implement SOP form


Use AND gate to implement POS form

### BCD to Seven Segment Decoder

Digital readouts found in electronic calculators and digital watches use LEDs. Each digit of the readout is formed from seven segments, each consisting of one LED that can be illuminated by digital signals.

A BCD-to-Seven segment decoder is a combinational circuit that accepts a digit in BCD and generates the appropriate o/p's for the selection of segments that display the digit.

 The seven outputs of the decoder (a, b, c, d, e, f, g) select the corresponding segments in the display as shown below.



Cell No.	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	1	0	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	1	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10, 11, 12, 13, 14, 15	All other i/p's				x	x	x	x	x	x	x



When we map all the seven segment variables into K-map individually, we get expressions as.

$$\begin{aligned} a &= w + y + xz + \bar{x}\bar{z} \\ b &= \bar{x} + \bar{y}\bar{z} + yz \\ c &= x + \bar{y} + z \\ d &= w + y\bar{z} + \bar{x}\bar{z} + \bar{x}y + x\bar{y}z \\ e &= y\bar{z} + \bar{x}\bar{z} \\ f &= w + \bar{y}\bar{z} + x\bar{y} + x\bar{z} \\ g &= w + x\bar{y} + \bar{x}y + y\bar{z} \end{aligned}$$

### Decoders with Enable Input

Observe that in the decoders dealt with so far, one of the o/p's is always '1' in the uncomplemented o/p version (active high o/p version) or one of the o/p is always '0' in the complemented o/p version (active low o/p version). There are several applications where we would want all the o/p's to be '0' or '1' respectively. This can be achieved by including an enable i/p to the decoder.


The enable i/p's are also useful in cascading decoders to increase their i/p-o/p lines.

For eg: In cascading 2:4 decoders to obtain 4:16 line decoder.

- Whenever enable pin is high (1), Decoder is said to be activated and it is enabled to perform operation.
- Whenever enable pin is low (0), Decoder is said to be de-activated and it is not-enabled to perform operation.


### 2:4 Decoder with Enable

Inputs			Outputs			
E	a <sub>1</sub>	a <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

fig(a): 2:4 line Active High o/p (Uncomplemented) Decoder.


Inputs			Outputs			
E	a <sub>1</sub>	a <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 

fig(b): 2:4 Active Low o/p (Complemented) Decoder.

One important application of a decoder is its use as a demultiplexer.

 
The i/p's of decoder acts as select lines of demux & enable of decoder acts as i/p line of demux.



Decoder as a Demultiplexer.



## 4:16 Decoder using 2:4 Decoders.

 

This 4:16 Decoder generates 16 minterms from  $\bar{a}_3 \bar{a}_2 \bar{a}_1 \bar{a}_0$  to  $a_3 a_2 a_1 a_0$ .

## ENCODERS

An encoder is a digital function that performs the inverse operation of a decoder.

An encoder has  $2^n$  input lines and 'n' output lines.

$$2^n \text{ inputs} = n \text{ outputs.}$$

$$\therefore (2^n : n)$$

Multi inputs = Multi outputs.

eg: 4:2 Encoder, 8:3 Encoder

8:3 Encoder ( $2^3 : 3$ ,  $n=3$ )


NOTE: Any one i/p will be high at an instant of time

Inputs								Outputs		
$x_0$	$x_1$	$x_2$	$x_3$	$x_4$	$x_5$	$x_6$	$x_7$	$y_2$	$y_1$	$y_0$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$y_2 = x_4 + x_5 + x_6 + x_7$$

$$y_1 = x_2 + x_3 + x_6 + x_7$$

$$y_0 = x_1 + x_3 + x_5 + x_7$$

 

There are some problems associated with encoders.

It is possible that when more than one inputs are at logic 1 (High) there may be an error in the output code.

For eg: if  $x_3 = x_4 = 1$ , then  $y_2, y_1, y_0 = 111$ , whereas this o/p should have resulted for only  $x_7 = 1$ .

The other problem is that the o/p is 000 when all the i/p's are at logic 0 (Low) as well as when  $x_0 = 1$ .

These problems can be overcome by the priority encoder with a validity indicator. The truth table of a 8:3 priority encoder is shown below.

Row No.	Inputs $x_0, x_1, x_2, x_3, x_4, x_5, x_6, x_7$								Outputs $y_2, y_1, y_0, \text{Valid}$			
0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	1
2	x	1	0	0	0	0	0	0	0	0	1	1
3	x	x	1	0	0	0	0	0	0	1	0	1
4	x	x	x	1	0	0	0	0	0	1	1	1
5	x	x	x	x	1	0	0	0	1	0	0	1
6	x	x	x	x	x	1	0	0	1	0	1	1
7	x	x	x	x	x	x	1	0	1	1	0	1
8	x	x	x	x	x	x	x	1	1	1	1	1

Observe in the table that higher order bits have higher priority. For eg: if  $x_3$  is at logic 1, then irrespective of the logic values of  $x_0, x_1$  &  $x_2$  the o/p code will be 011. The valid o/p being '1' indicates that the i/p code is valid.

The row 0 & row 1 o/p's are now distinguished by the logic level of the 'Valid' output.


Exercise: Write the condensed truth table for 4:2.

priority encoder with a valid o/p where the highest priority is given to the highest bit position or input with highest index and obtain the minimal sum expressions for the o/p's.

Sol<sup>n</sup>

Cell No.	$x_0$	$x_1$	$x_2$	$x_3$	$y_1$	$y_0$	Valid
0	0	0	0	0	0	0	0
8	1	0	0	0	0	0	1
4, 12	x	1	0	0	0	1	1
2, 6, 10, 14	x	x	1	0	1	0	1
1, 3, 5, 7, 9, 11, 13, 15	x	x	x	1	1	1	1

 Let us now construct the K-maps for the o/p's.



Exercise: 4:2 priority encoder with highest priority to the lowest significant i/p or lower index.

So | 2

Cell No.	$x_0$	$x_1$	$x_2$	$x_3$	$Y_1$	$Y_0$	Valid
0	0	0	0	0	0	0	0
15, 8, 9, 10, 11, 12, 13, 14	1	X	X	X	0	0	1
4, 5, 6, 7	0	1	X	X	0	1	1
2, 3	0	0	1	X	1	0	1
1	0	0	0	1	1	1	1

After constructing K-maps for outputs, we get minimal sum expressions as

$$Y_1 = \bar{x}_0 \bar{x}_1 x_2 + \bar{x}_0 \bar{x}_1 x_3$$

$$Y_0 = \bar{x}_0 x_1 + \bar{x}_0 \bar{x}_2 x_3$$

$$\text{Valid} = x_0 + x_1 + x_2 + x_3$$

## PARITY CIRCUITS (Generator & Checker)

A parity bit is an extra bit included with a binary message to make the no. of 1's either odd or even.

The message, including the parity bit, is transmitted and then checked at the receiving end for errors.

An error is detected if the parity of the data bits in the message does not correspond to the parity bit transmitted.

The circuit that generates the parity bit in the transmitter is called a PARITY GENERATOR

The circuit that checks the parity bit in the receiver is called a PARITY CHECKER

### Even Parity Generator

Consider a 3-bit message to be transmitted with an even parity bit.

Row No.	3-bit Message			Parity Bit
	X	Y	Z	P
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

P.T.O




From truth table, 3 bits X, Y & Z constitute the message and are the inputs to the circuit.

The parity bit, P is the output.

For even parity, the bit 'P' must be generated to make the total number of 1's (including P) even.

X \ YZ	00	01	11	10
0	0 <sup>0</sup>	1 <sup>1</sup>	0 <sup>3</sup>	1 <sup>2</sup>
1	1 <sup>4</sup>	0 <sup>5</sup>	1 <sup>7</sup>	0 <sup>6</sup>
 
$$P_{\text{even}} = X \oplus Y \oplus Z$$



### Odd Parity Generator

3-bit message to be transmitted with an odd parity bit


Row No.	3-bit Message			Parity Bit P
	X	Y	Z	
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

P.T.O

From truth table, for odd parity, the bit 'P' must be generated to make the total no. of 1's (including P) odd.

X \ YZ	00	01	11	10
0	1 <sup>0</sup>	0 <sup>1</sup>	1 <sup>3</sup>	0 <sup>2</sup>
1	0 <sup>4</sup>	1 <sup>5</sup>	0 <sup>7</sup>	1 <sup>6</sup>

$$P_{\text{odd}} = (X \odot Y) \oplus Z$$

 

The 3-bits in the message, together with the parity bit, are transmitted to their destination, where they are applied to a parity checker circuit to check for possible errors in the transmission.

The information transmitted with even parity (odd parity), the 4 bits received must have an even (odd) no. of 1's.

An error occurs if these bits have an odd (even) no. of 1's, indicating that at least one bit has changed its value during transmission.

If such error occurs, the o/p of the parity checker will be equal to 1.

P.T.O




## Even Parity Checker

Row No.	4-bit Information (3 bit + 1 bit P)				C
	X	Y	Z	P	
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	0

XY \ ZP				
	00	01	11	10
00	0 <sup>0</sup>	1 <sup>1</sup>	0 <sup>3</sup>	1 <sup>2</sup>
01	1 <sup>4</sup>	0 <sup>5</sup>	1 <sup>7</sup>	0 <sup>6</sup>
11	0 <sup>12</sup>	1 <sup>13</sup>	0 <sup>15</sup>	1 <sup>14</sup>
10	1 <sup>8</sup>	0 <sup>9</sup>	1 <sup>11</sup>	0 <sup>10</sup>
 
$$C_{\text{even}} = X \oplus Y \oplus Z \oplus P$$



Here, if  $C=0 \rightarrow$  no errors, if no. of 1's in the stream (XYZP) are even.


&  $C=1 \rightarrow$  error, if no. of 1's in the stream (XYZP) are odd.

## Odd Parity Checker

Row No.	4 bit Information (3 bit + 1 bit P)				C
	X	Y	Z	P	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	1

XY \ ZP				
	00	01	11	10
00	1 <sup>0</sup>	0 <sup>1</sup>	1 <sup>3</sup>	0 <sup>2</sup>
01	0 <sup>4</sup>	1 <sup>5</sup>	0 <sup>7</sup>	1 <sup>6</sup>
11	1 <sup>12</sup>	0 <sup>13</sup>	1 <sup>15</sup>	0 <sup>14</sup>
10	0 <sup>8</sup>	1 <sup>9</sup>	0 <sup>11</sup>	1 <sup>10</sup>
 
$$C_{\text{odd}} = (X \oplus Y) \odot (Z \oplus P)$$




Here if  $C=0 \rightarrow$  no errors, if no. of 1's in the stream (XYZP) are odd.

&  $C=1 \rightarrow$  error, if no. of 1's in the stream (XYZP) are even.

Exercise: Construct 3:8 Decoder using 2:4 decoders.

Soln

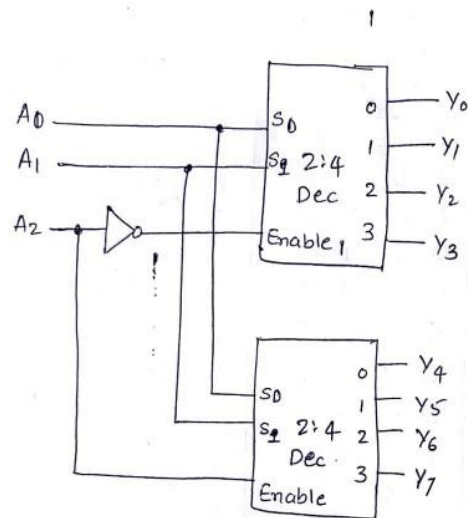


$A_2$	$A_1$	$A_0$	$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

## COMPARATORS

Comparators are designed to compare the magnitude of two binary number and indicate whether one is greater than, less than or equal to the other.

### One Bit (1-Bit) Comparator

 

$$(A > B) = 1 \text{ if } a > b$$


$$(A = B) = 1 \text{ if } a = b$$

$$(A < B) = 1 \text{ if } a < b$$


a	b	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

$$\therefore (A > B) = \bar{a}b, (A = B) = \bar{a}\bar{b} + ab, (A < B) = a\bar{b}$$

$$= a \oplus b$$

 

## 2-bit Comparator

 


$(A > B) = 1$  if  $a_1 a_0 > b_1 b_0$


$(A = B) = 1$  if  $a_1 a_0 = b_1 b_0$

$(A < B) = 1$  if  $a_1 a_0 < b_1 b_0$

Cell no.	$a_1$	$a_0$	$b_1$	$b_0$	$A > B$	$A = B$	$A < B$
0	0	0	0	0	0	1	0
1	0	0	0	1	0	0	1
2	0	0	1	0	0	0	1
3	0	0	1	1	0	0	1
4	0	1	0	0	1	0	0
5	0	1	0	1	0	1	0
6	0	1	1	0	0	0	1
7	0	1	1	1	0	0	1
8	1	0	0	0	1	0	0
9	1	0	0	1	1	0	0
10	1	0	1	0	0	1	0
11	1	0	1	1	0	0	1
12	1	1	0	0	1	0	0
13	1	1	0	1	1	0	0
14	1	1	1	0	1	0	0
15	1	1	1	1	0	1	0

 
 
$$(A > B) = a_0 \bar{b}_1 \bar{b}_0 + a_1 \bar{b}_1 + a_1 a_0 \bar{b}_0$$



$$(A < B) = \bar{a}_1 \bar{a}_0 b_0 + \bar{a}_0 b_1 b_0 + \bar{a}_1 b_1$$

$$(A > B) = \sum m(4, 8, 9, 12, 13, 14)$$


$$(A < B) = \sum m(1, 2, 3, 6, 7, 11)$$

$$(A = B) = \sum m(0, 5, 10, 15)$$

We observe that  $(A = B)$  minterms are the uncovered minterms of  $(A > B)$  &  $(A < B)$ .

$$\therefore (A = B) = \text{Complement of } [A > B + A < B]$$
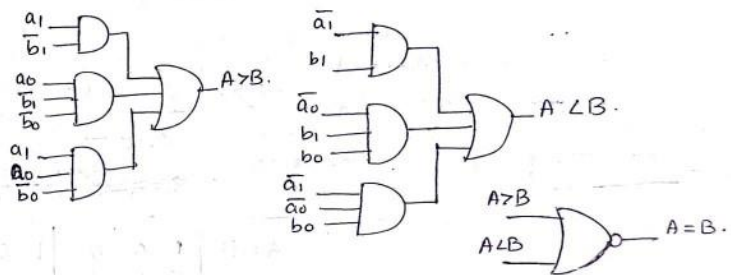
$$\therefore (A = B) = \overline{(A > B) + (A < B)}$$






Most often there is a requirement to compare two 4-bit, 8-bit or higher bit binary numbers.

It is worthwhile to look at a 1-bit comparator with inputs and outputs which can be used to cascade several of these to configure multiple-bit comparators.

 The block diagram of 1-bit comparator at  $i$ th stage, of such a cascade is shown below.



$x_i = A > B$ ,  $y_i = A = B$ ,  $z_i = A < B$  of previous stage


$x_{i+1} = A > B$ ,  $y_{i+1} = A = B$ ,  $z_{i+1} = A < B$  of next stage

Note: Any one of  $(x, y, z)$  will be high at an instant of time.

No two of them will be high at an instant of time.


If such condition occurs, the outputs are don't care conditions.

#### 4 Bit Comparator

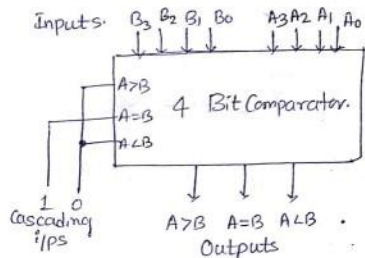

Comparing i/p A, B	Cascading i/p A > B, A = B, A < B			Outputs A > B, A = B, A < B		
A > B	0	1	0	1	0	0
A = B	0	1	0	0	1	0
A < B	0	1	0	0	0	1
A = B	1	0	0	1	0	0
	X	1	X	0	1	0
	0	0	1	0	0	1
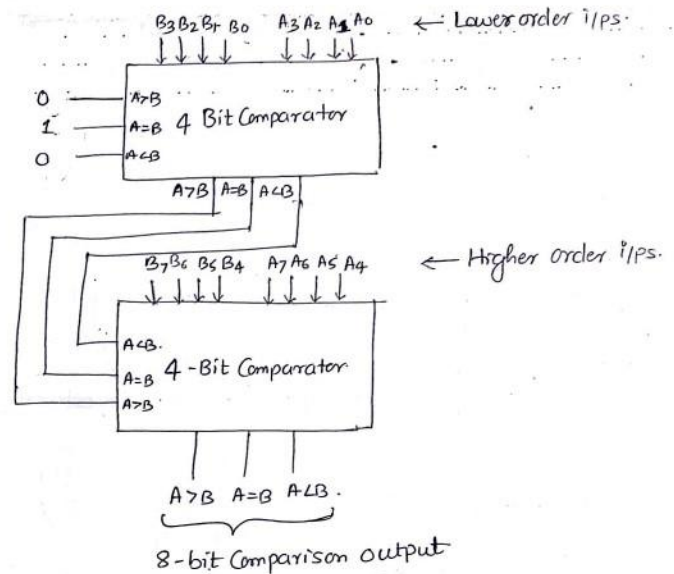
#### 8-bit Comparator Using 4-bit Comparator



When Higher order bits of A & B are different, we can directly say that  $(A > B)$  or  $(A < B)$ . Here it doesn't care about the lower order bit and also the cascading i/p's it's getting.

When Higher order bits of A & B are same, at that time Comparator compares the lower order bits of A & B and according to that it says output  $(A = B)$ .

The final 8-bit Comparator o/p will be the cascading inputs values.

Comparing i/p A, B	Cascading i/p A > B, A = B, A < B			Outputs A > B, A = B, A < B			
A < B	A > B	X	X	X	1	0	0
A = B	A > B	X	1	X	0	1	0
	A < B	0	0	1	0	0	1
	A < B	1	0	0	1	0	0
	A < B	0	0	0	1	0	1
	A < B	1	0	0	0	0	1